INDEX

S. No.	Date	Name of the Experiment	Page No.	Marks Awarded	Signature
1	21/1/2026	Verification of Kirchoff's Voltage Law and Kirchoff current Law	99		
2	28/1/2026	Open circuit and load Characteric of DC Shunt generator	99		
3	~~04~~ 11/2/2026	Staircase Wiring	99		
4	18/02/26	Half wave and Full wave Rectifier	100		
5.	25/2/26	Zener diode as voltage Regulation	100		
6.	11/03/26	characteristic of LVDT Characteristic variable different Transformer.	100		

Completed 11/03/2026

Staircase wiring

Circuit Diagram

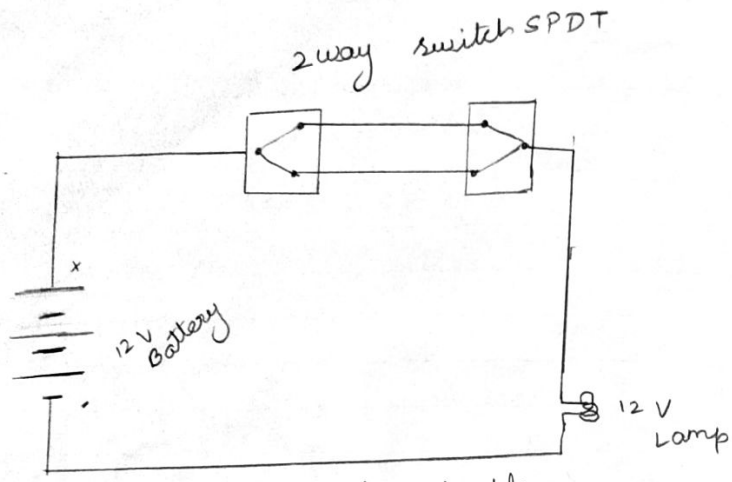

single pole double Throw switch

S.NO	S_1	S_2	Lamp
1	on	On	on
2	on	off	off
3	off	on	off
4	off	off	on

component	proteus	specify -cation
Ac supply	Vsine	Applicat -ion 230V
Two-way switch	SPDT	Frequen -cy 50Hz
Lamp	Ammeter	230 V

Staircase Wiring

Aim

To develop and test the staircase wiring using proteus

Apparatus Required

Laptop with protues software

Theory:

Staircase wiring is a common multiple way switching or two way ~~stw~~ switching connection. It is values wiring for one light with two switches In this set up is controlled by two switches. In ~~this~~ ~~s~~ located operated the load. from separated position above or below the staircase from inside or outside of room or two way led switch

Procedure

Drag the required componets from the process libary

connect the component as

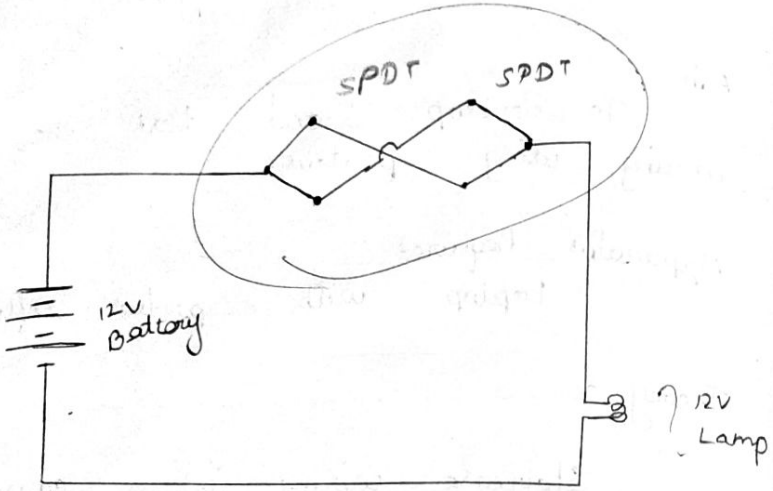

Mode	S_1	S_2	Lamp
1	on	on	off
2	on	off	on
3	off	on	on
4	off	off	off

* Run the simulation and check the lamp for different switch condition

SAVEETHA
ENGINEERING COLLEGE
SAVEETHA NAGAR 602 105
BE THE BEST

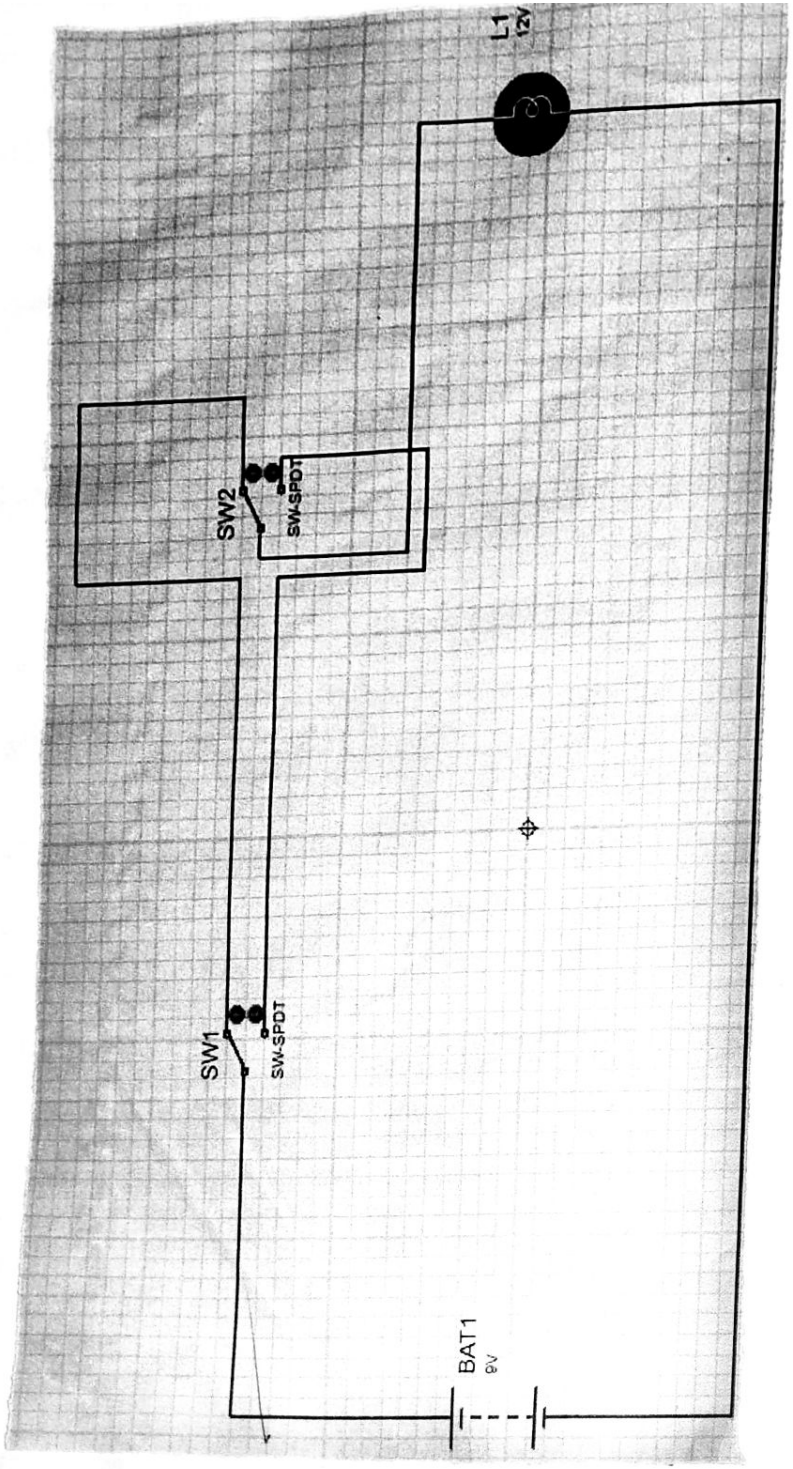

99

25/02/22

Result :

Thus the staircase using connection were developed and tested successfully

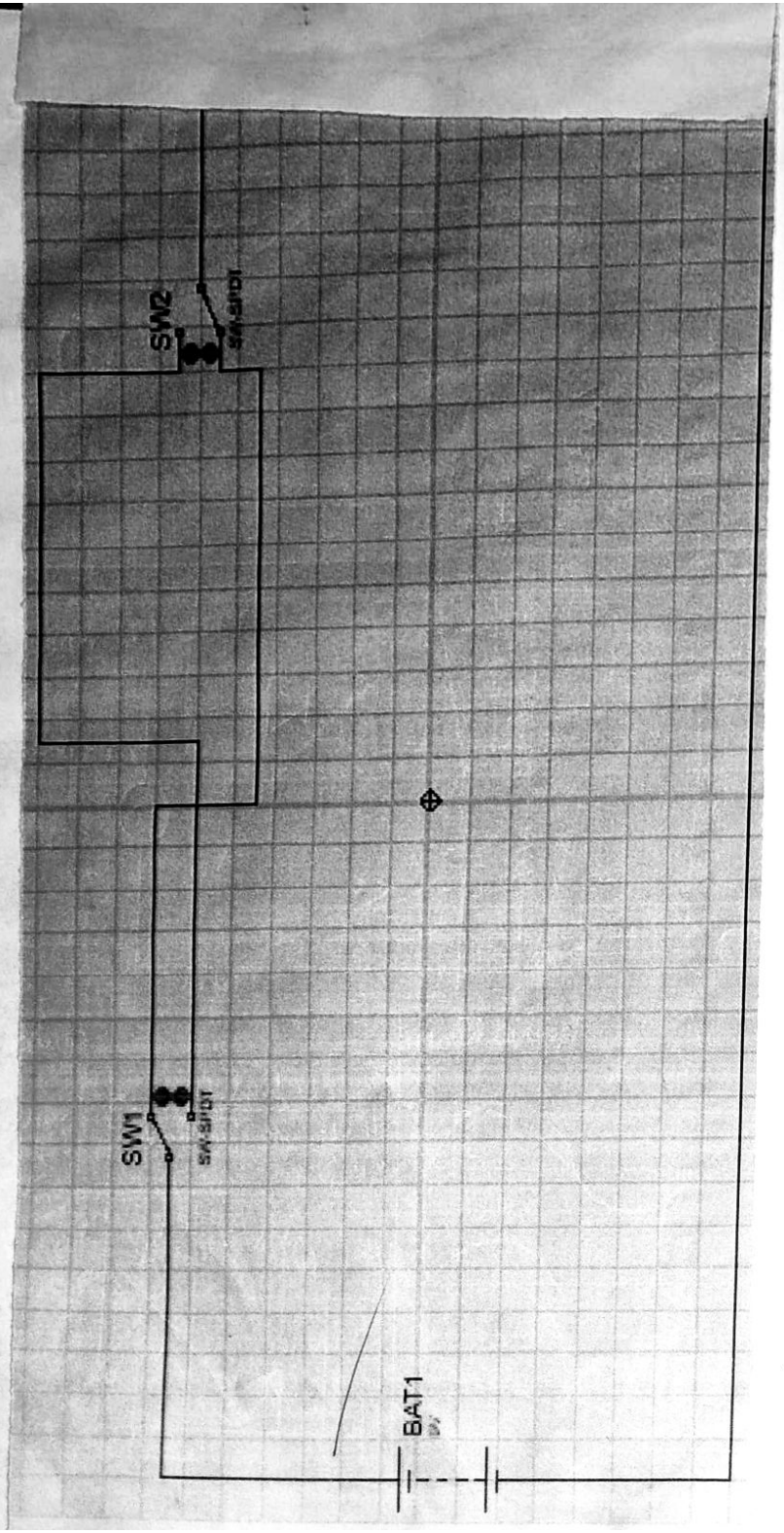

SAVEETHA
ENGINEERING COLLEGE
SAVEETHA NAGAR 602 105
BE THE BEST